


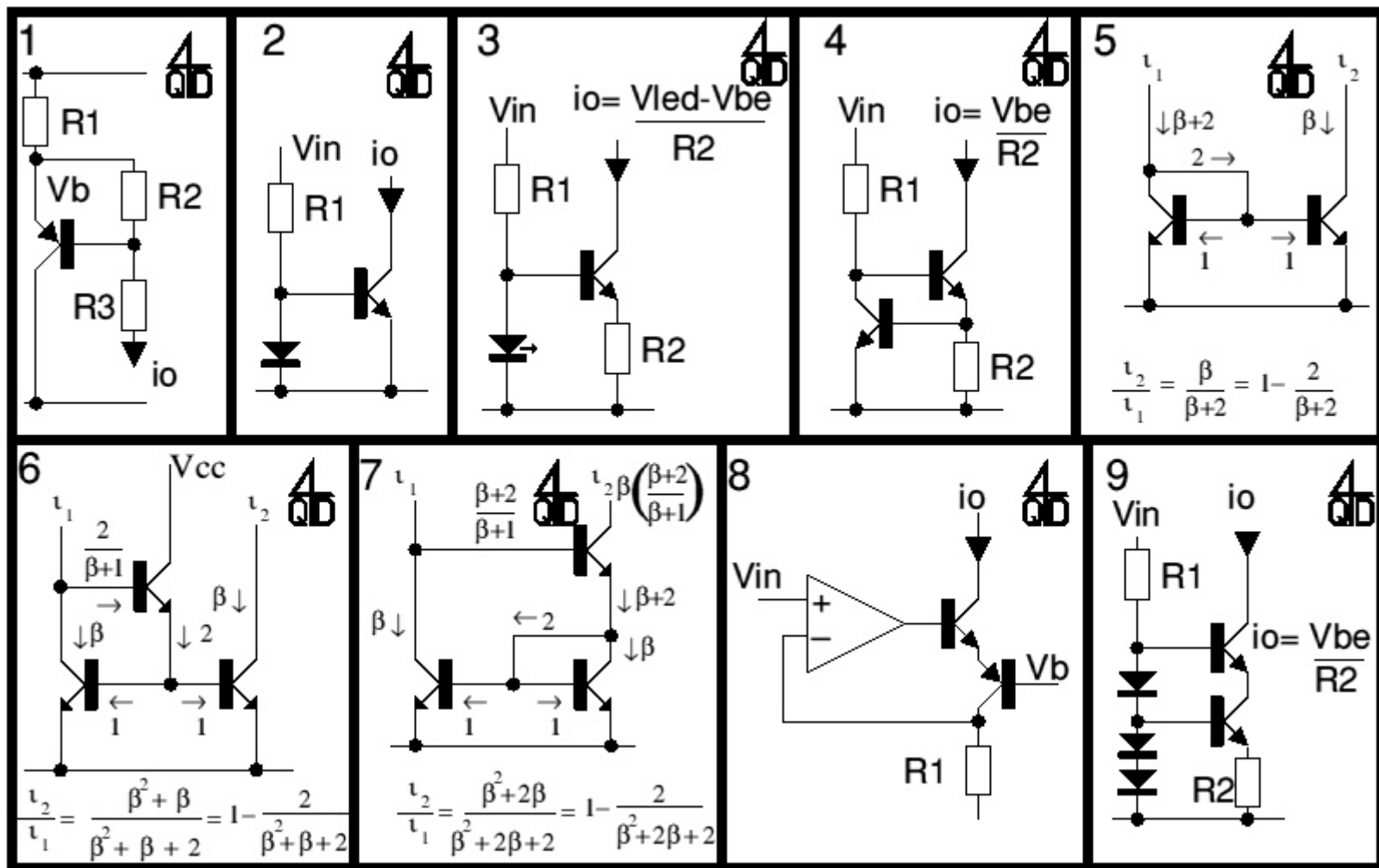


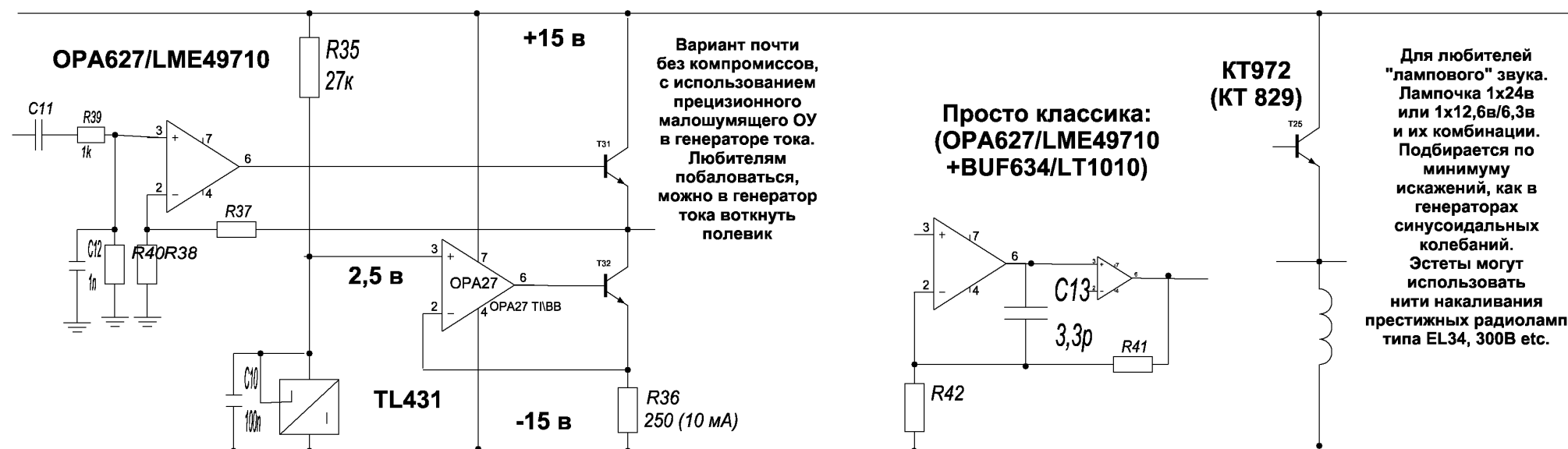

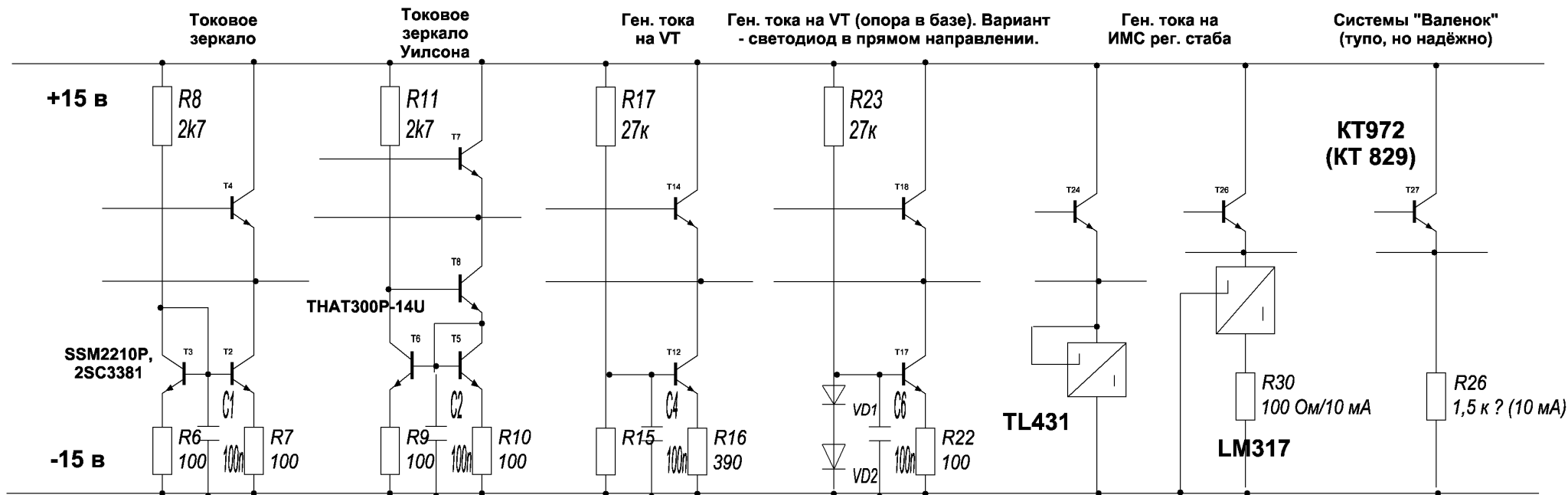
БУФЕРНЫЕ КАСКАДЫ предварительных усилителей с ОУ в классе А от Самосбора



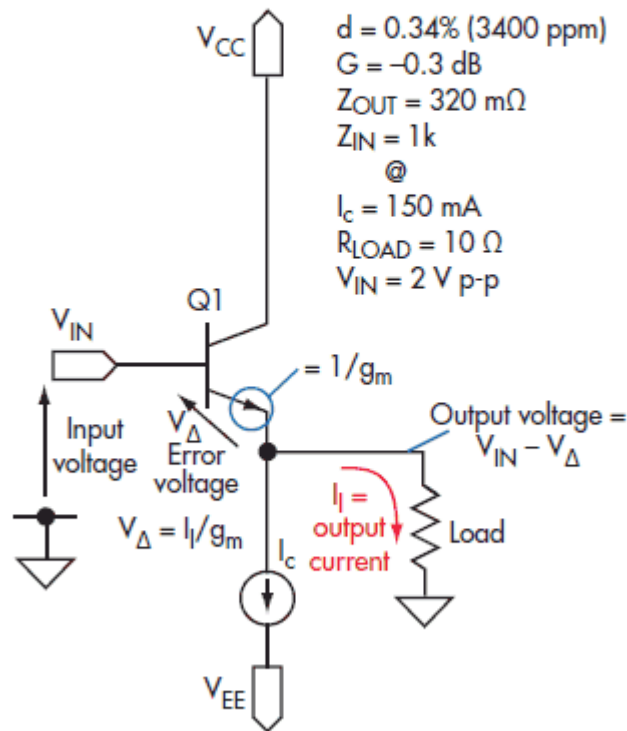The classic emitter-follower circuit (a) creates a nonlinear error voltage that reduces gain below unity. A triplet of devices (b) can compensate for this error as well as secondary effects.




(a) Basic follower

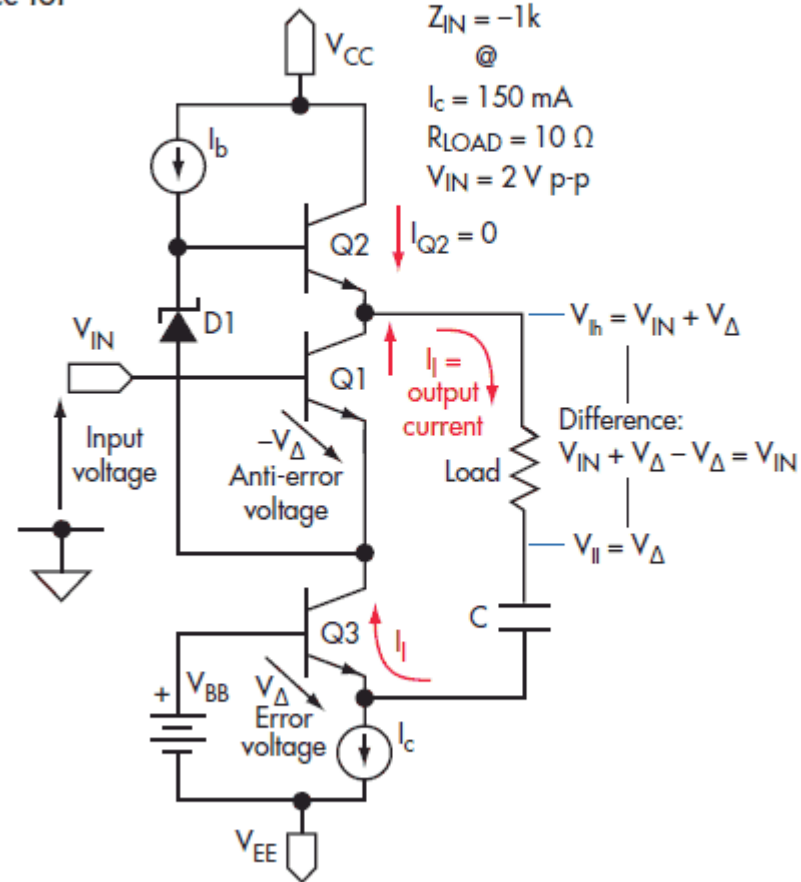

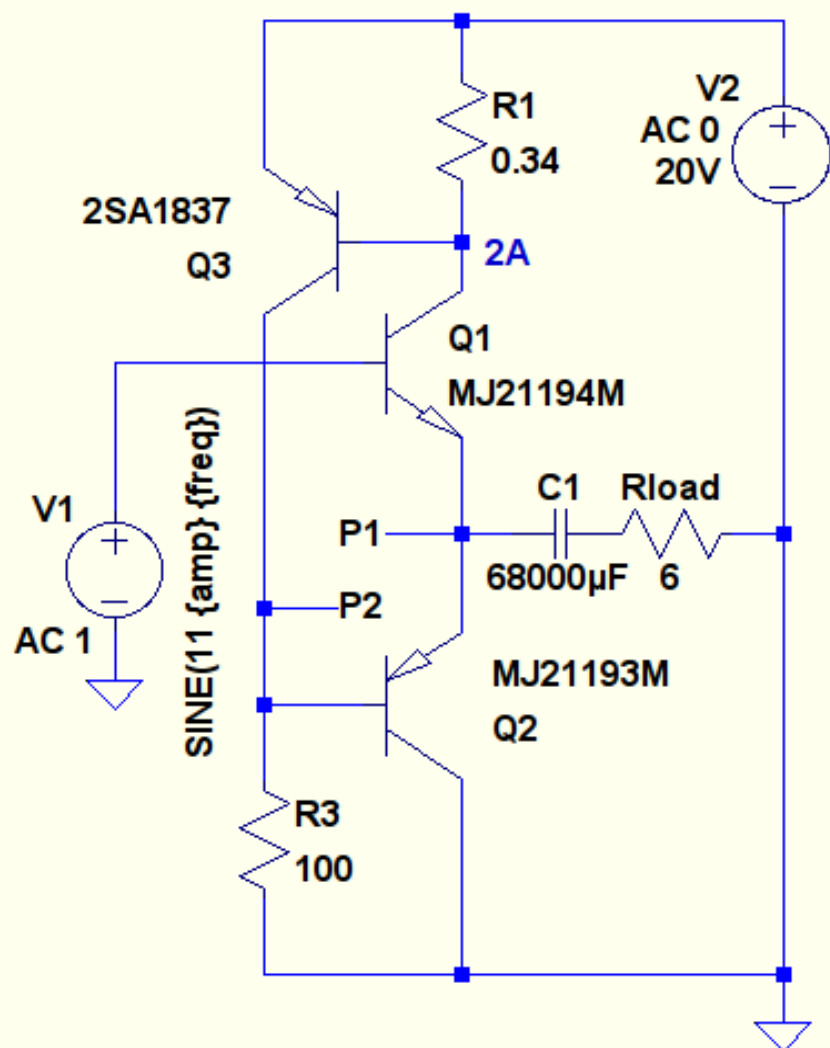(b) Tringlotron

dee01.asc

```
.param plotwinsize=0 freq = 1K amp = 7.0
;step temp 20 50 1
.tran 0 {100/freq} {80/freq} {0.005/freq}
;ac oct 256 0.1 20K
;.op
```



01.raw

